



# **Bangladesh University Of Business & Technology (BUBT)**

## **DEPARTMENT OF COMPUTER SCIENCE & ENGINEERING**

**Faculty of Engineering**

**07 August ,2021.**

# Project Report

## On

Design a simplified circuit from a given circuit (which consists of two independent sources) which provides the same value of power to the load.

## Submitted To

Mohammad Nowshed Al Nur

Lecturer

Department of EEE, BUBT

Submitted By,

| <i>Name</i>                  | <i>ID</i>   | <i>Intake/Section</i> |
|------------------------------|-------------|-----------------------|
| Hamim Sheikh                 | 20215103049 | 47/1                  |
| MD EHTA SHAMUL<br>ISLAM SHAD | 20215103041 | 47/1                  |
| Amzad Hossain                | 20215103048 | 47/1                  |
| Ritu Khatun                  | 20215103031 | 47/1                  |
| Sumaiya Akter<br>Nurjahan    | 20215103042 | 47/1                  |

**Dedicated to**

Our Parents

&

Honorable Teacher

# **ACKNOWLEDGEMENT**

We appropriate my thankfulness and sincere thanks to my teacher Mohammad Nowshed Al Nur ,  
Department of Electrical and Electronics Engineering  
for his Generous Efforts and keep following Which has  
Remained as a valuable asset for the successful of our  
project report .We Acquire knowledge how to solve  
Circuit . when we work for this project we have faces  
many problems and we discuss our teammates and  
course teacher. Our Project Teacher gladly help us to  
done this project. Then we Done this Project and  
achieve success.

# **Table of Contents**

- i. Chapter – 1 :  
Project Title, Student(s) name and ID  
with department name & BUBT logo
- ii. Chapter – 2 :  
Introduction
- iii. Chapter – 3 :  
Background, Motivation
- iv. Chapter – 4 :  
Literature Review  
Proposed method  
Methodology
- v. Chapter – 5 :  
Simulation / Hardware Prototype
- vi. Chapter – 6 :  
Results
- vii. Chapter – 7 :  
Conclusion , References

# Introduction

The Thevenin's theorem states that any linear two terminal circuit consisting of sources and resistors connected to a given load  $R_L$  can be replaced by an equivalent circuit consisting a single voltage source of magnitude  $V_{th}$  with a series resistance  $R_{th}$  across the terminal of  $R_L$ .

The Thevenin's model of two terminal network where the current through the load is same therefore, these two circuits are equivalent to each other.

# Background

Load resistance is a circuit or a simply way to saying that load resistance is what through which you consume power .To calculate Thevenin's resistance and voltage we need to find the power source in the original circuit and remove them and calculating total resistance between the open connection points .Draw the Thevenin equivalent circuit, with the Thevenin voltage source in the series with the Thevenin's calculating total resistance between the open connection points. Draw the Thevenin equivalent Circuit, with the Thevenin voltage source in the series with the Thevenin's resistance. To calculate load current we need to find the total current flowing through by using the Ohm's Law,  $I = V_{th}/R_{th}$  .


## Motivation

Thevenin's Theorem are used where the load can be Varied . So, basically these methods reduce the big linear circuit into 1 source & 1 resistor. Later we can put any kind of load & measure the variations of current & voltages across the load. The load can be a Fan, bulb, etc.



# Literature Review

Thevenin's theorem provides a technique by which the fixed part of the circuit is replaced by an equivalent circuit. According to Thevenin's theorem, the linear circuit in Fig. 4.23(a) can be replaced by that in Fig. 4.23(b). (The load in Fig. 4.23 may be a single resistor or another circuit.) The circuit to the left of the terminals in Fig. 4.23(b) is known as the Thevenin equivalent circuit; it was developed in 1883 by M. Leon Thevenin (1857–1926), a French telegraph engineer.

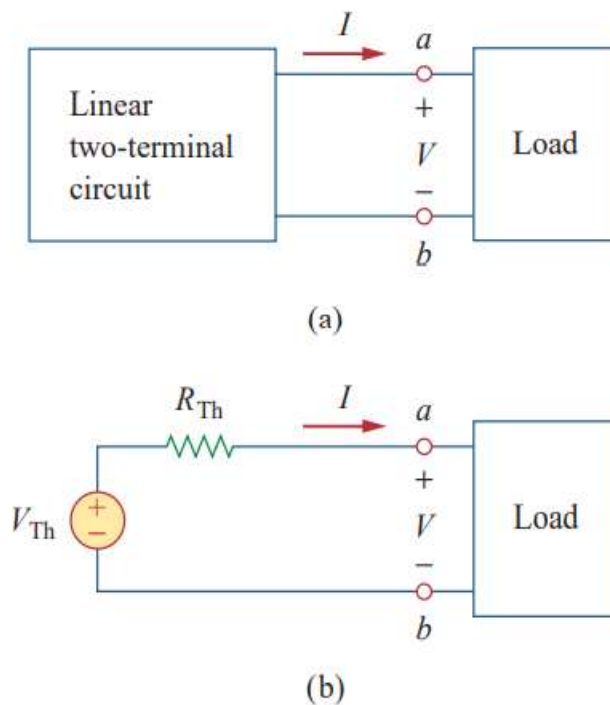

**Figure 4.23**

## Proposed Methodology

At first , we select a Thevenin's Theorem Circuit .That has a two independent source , one is current source & another one is voltage source & also take resistance and load resistance . We Draw a circuit . At last , we get  $V_{th}$  and  $R_{th}$  step by step processing the calculation with Thevenin's theorem.

Thevenin's theorem states that a linear two-terminal circuit can be replaced by an equivalent circuit consisting of a voltage source  $V_{th}$  in series with a resistor  $R_{th}$ , where  $V_{th}$  is the open-circuit voltage at the terminals and  $R_{th}$  is the input or equivalent resistance at the terminals when the independent sources are turned off.


When We Calculate  $R_{th}$  we short the voltage source & current source & load resistance remove . For  $V_{th}$  we remove load resistance and applying KCL node 1 & node 2 . Then we get  $V_{th}$  Calculating the equation.

## Methodology


1. Connect to the circuit Diagram.
2. Measure current in  $R_L$ .
3. Connect the circuit.
4. Measure open circuit voltage  $V_{oc}$  by open circuiting terminals I,  $R_{th}$ ,  $V_{th}$ .
5. Draw the Thevenin's equivalent circuit .
6. Measure current flows .

# Simulation

For  $V_{th}$  :

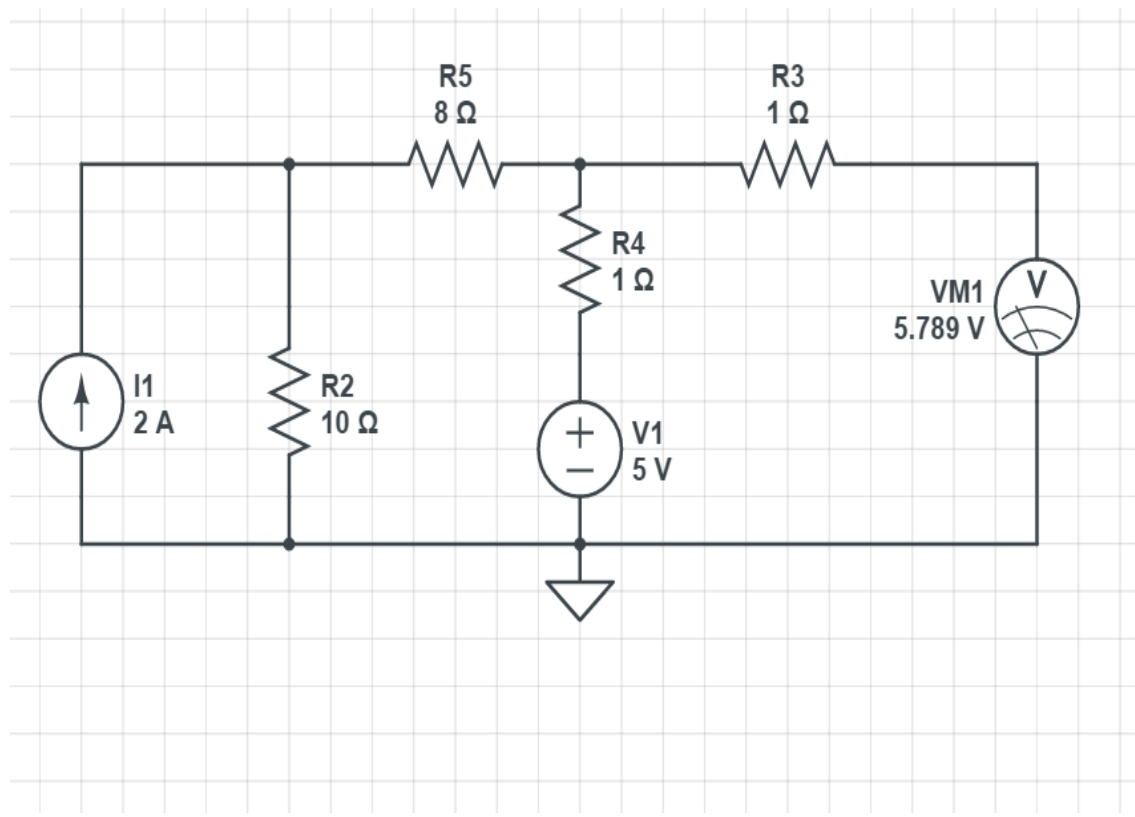

For  $R_{th}$  :

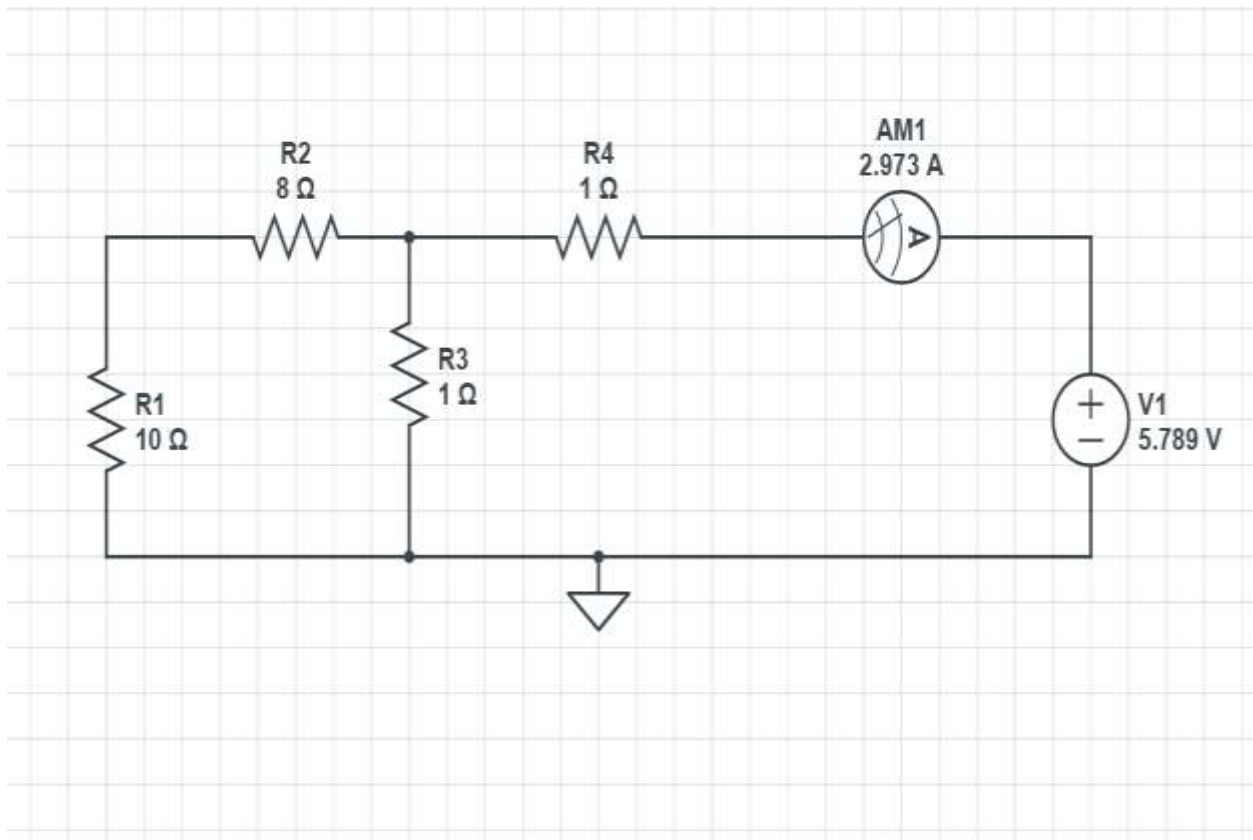

$$R_{th} = v_{th}/i$$

$$=(5.789/2.973)$$

$$= 1.94$$

# Result

Circuit Diagram :

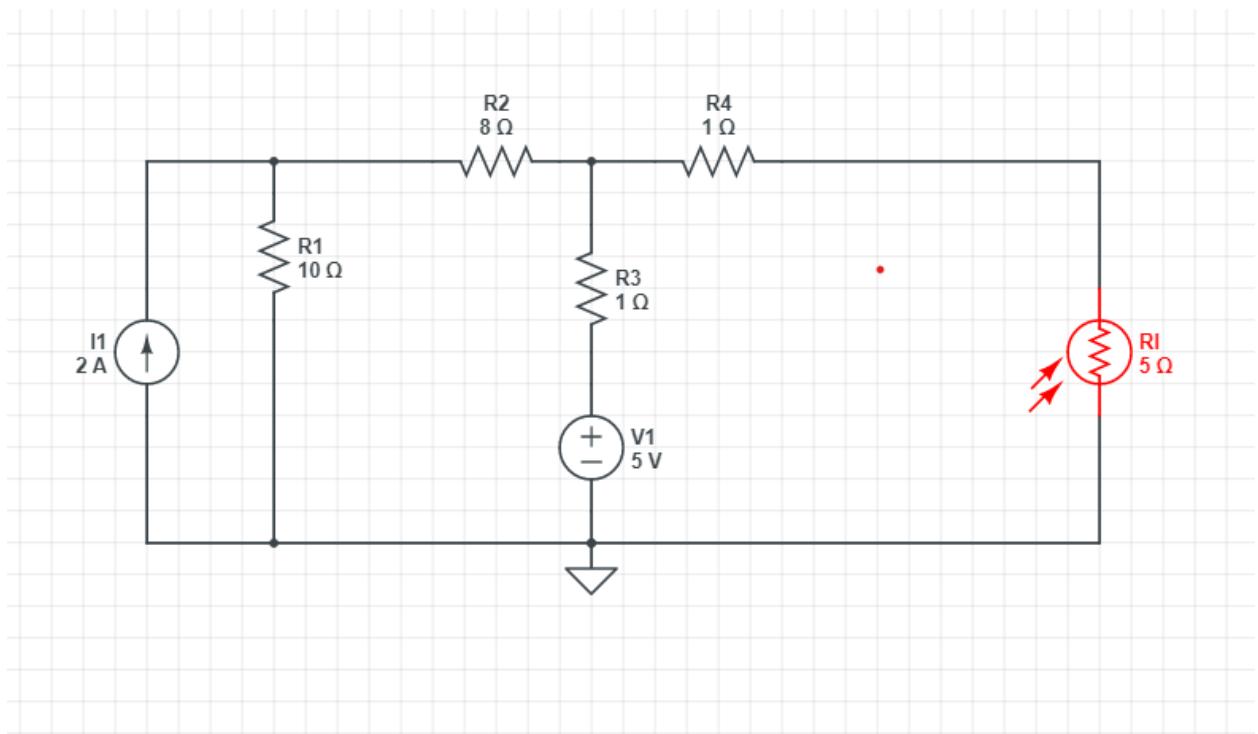


Figure – 01

Finding  $R_{th}$  :

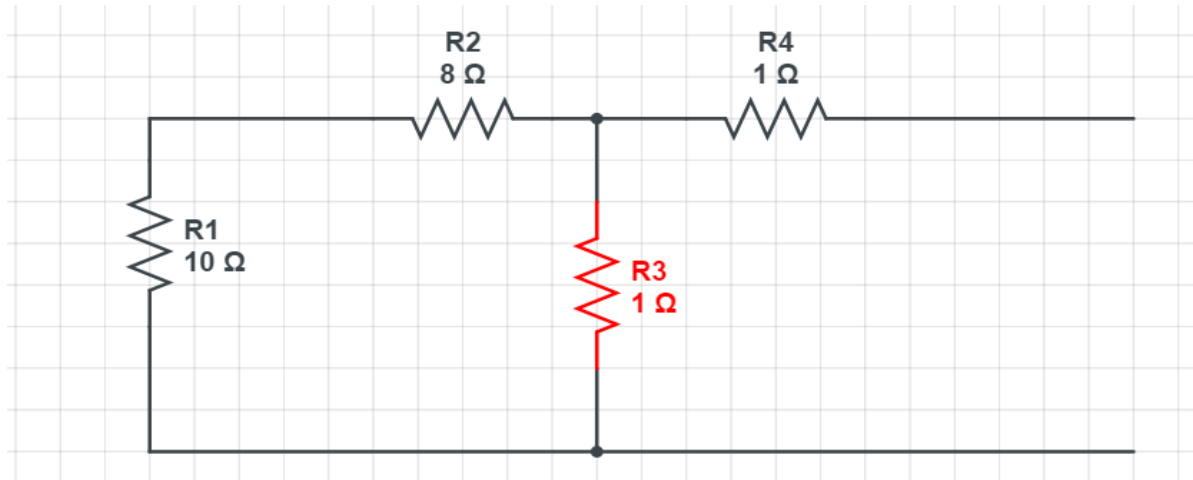


Figure -02

$$R = (R1 + R2) = (10 + 8) \Omega$$

$$= 18 \Omega$$

$$R' = (R \parallel R3) = 18 * 1 / 18 + 1 = 18 / 19 \Omega$$

$$R'' = (R' + R4) = 18 / 19 + 1 = 1.94 \Omega$$

Finding  $V_{th}$  :

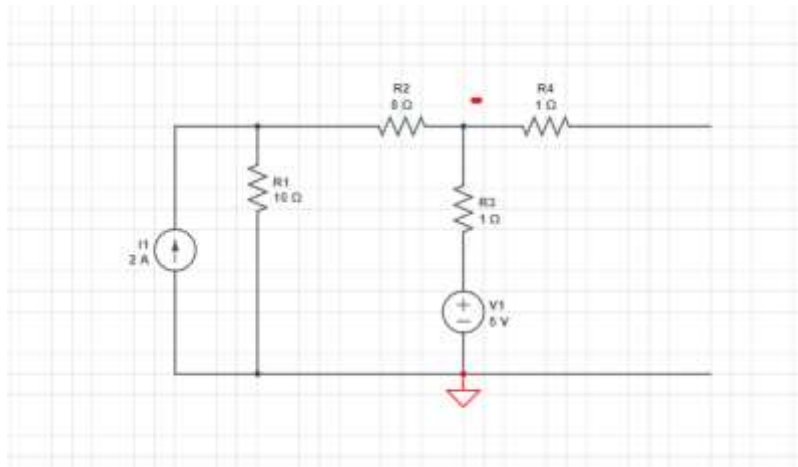


Figure -03

Applying KCL At Node 1,

$$2 = (v1 - v3)/10 + (v1 - v2)/8$$

$$2 = (v1 - 0)/10 + (v1 - v2)/8$$

$$20 = v1 + 1.25v1 - 1.25v2$$

$$20 = 2.25v1 - 1.25v2 \text{ -----(1)}$$

Applying KCL At node 2,



$$(v_1 - v_2)/8 = (v_2 - 5)/1$$

$$V_1 - v_2 = 8v_2 - 40$$

$$V_1 - 9v_2 = -40 \text{ -----(2)}$$

Form Equation (1) & (2) Calculating,

$$V_1 = 12.105 \text{ V}$$

$$V_2 = 5.789 \text{ V}$$

We Know  $V_{th} = V_2$ .

$$\text{So, } V_{th} = V_2 = 5.789 \text{ V}$$

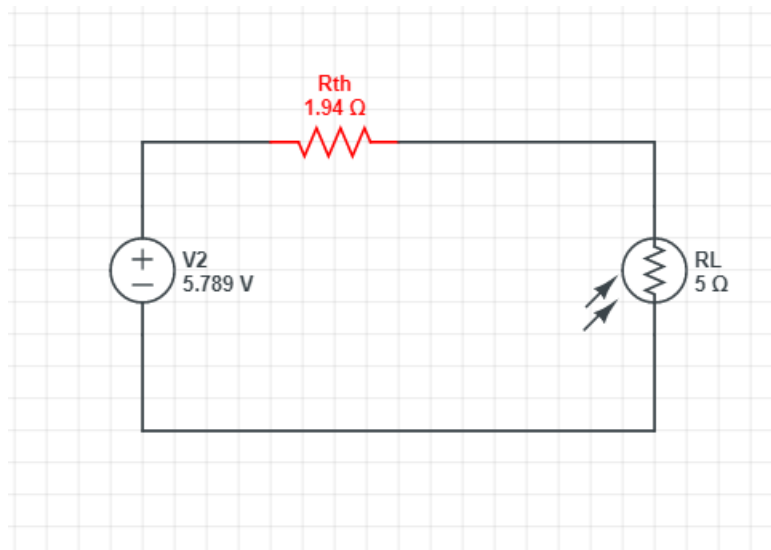


Figure - 04

$$\text{Finding } I_L = V_{th}/R_{th} = 5.789/1.94 = 2.98$$

## Conclusion

First we are afraid & Nervous about the project topic Thevenin's theorem method. But when we discuss our teammates & also helping our course teacher. Our course teacher cordially help us to solve this project. We discussing this project to our teammates so that this is too much easy to solve this project. when we solve the Circuit we get  $V_{th}$  &  $R_{th}$  Final value. Using Simulation we get  $V_{th}$  and  $R_{th}$  and this value is same then our teammates get satisfaction. In Next time any Thevenin's theorem circuit we can easily solve.

**Thank You**

## **References**

Fundamentals of Electric Circuit ,Fourth Edition,  
Matthew N.O.Sadiku , Charles Alexander ,page-139